

CS132 Quizzes - Digital Logic

May 2021

Josh Fitzmaurice

- 1 Subtract 9 from 13 in 8-bit wide two's complement.**

13 = 00001101
9 = 00001001
flip bits
= 11110110
add 1
-9 = 11110111
13 + (-9) = 00001101 + 11110111 = (1)00000100
ignore the overflow
13 - 9 = 00000100 = 4.

- 2 Explain, with the aid of a diagram, the difference between combinatorial and sequential logic circuits.**

A combinatorial logic will give the same results given the same inputs every time. There is no state of the circuit that can affect the output.

Whereas a sequential logic circuit can have a state which the circuit is in that could mean given the same input at different times could give a different result.

- 3 Show the truth table for an OR gate.**

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

Table 1: OR

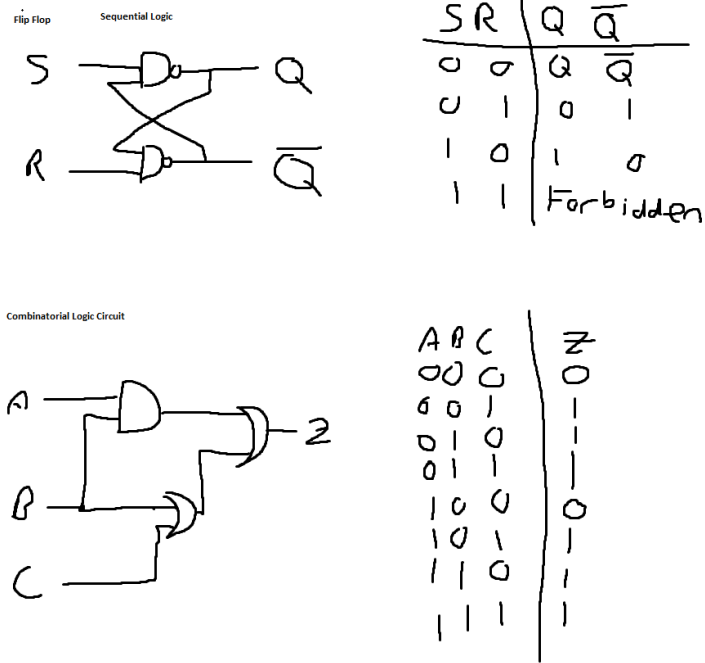


Figure 1: examples

4 Show the truth table for an XOR gate.

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

Table 2: XOR

5 Design a circuit that implements the function of an EX-OR gate using only NOT, AND and OR gates.

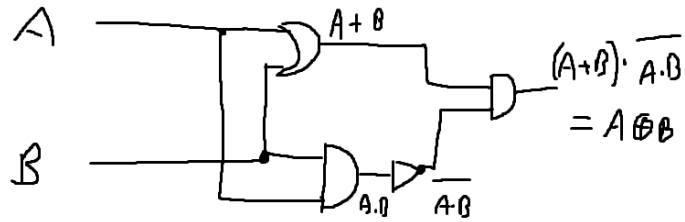


Figure 2: examples

6 Show the truth tables for a AND gate.

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

Table 3: AND

7 Design a circuit that implements the function of an OR gate using only NAND gates.

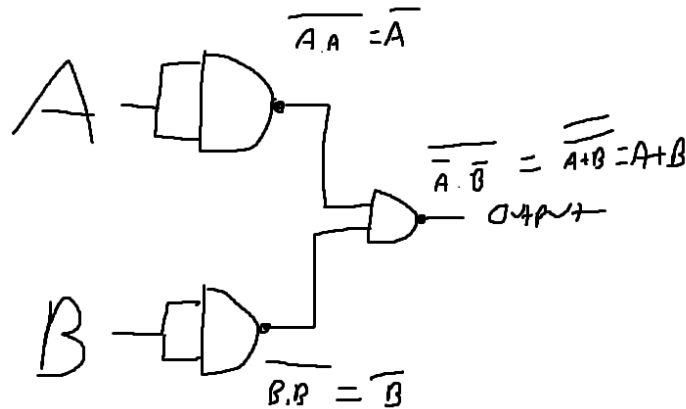


Figure 3: examples

8 Show the truth table for a 1-bit full adder.

A	B	Carry In	Sum	Carry Out
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

Table 4: 1-bit full adder truth table

9 Design an N-bit Full Adder circuit.

10 Explain how an N-bit Full Adder circuit can be modified to form an N-bit subtractor circuit.

We can use the fact that $a-b = a+(-b)$ and have a mode control line (z) that can turn b into -b.

This can be done by flipping the bits of b and then adding 1. So we can

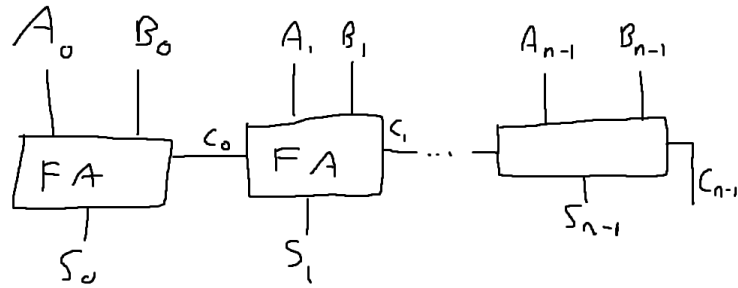


Figure 4: examples

XOR each B in b with the control line. When z is high the bits will be flipped, otherwise they will remain the same. Then to add the extra bit we can just use z as the Carry In to the first 1-bit full adder.

11 Design an N-bit Subtractor circuit.

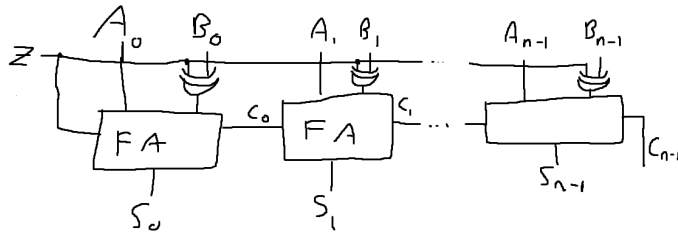


Figure 5: examples

12 Explain the function of a decoder, giving an example of where a decoder might be used.

A decoder turns n inputs into 2^n outputs. A decoder turns one of the outputs on determined by the binary value of the input.
 e.g. for an active-low decoder the truth table will be as follows:

x_0	x_1	y_0	y_1	y_2	y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Table 5: decoder

Decoders are often used to address unique memory locations in a microprocessor system

13 Explain the function of a multiplexer, giving an example of where a multiplexer might be used.

A multiplexer turns n inputs into 1 output, determined by some control modes. A multiplexer turns the output into one of the inputs determined by the control modes.

multiplexer truth table for a 4-1 multiplexor (inputs are x_0, x_1, x_2, x_3 and control signals are S_0, S_1):

S_0	S_1	output
0	0	x_0
0	1	x_1
1	0	x_2
1	1	x_3

Table 6: multiplexer

multiplexers are used for source selection control e.g. home stereo control.

14 Explain, using an appropriate truth table or circuit diagram, the operation of a D-Type latch.

A D-Type latch is essentially 1 bit of memory. Depending on the current state of the D-Type latch the input to the d-type latch will alter the output.

Below is the circuit diagram of a D-Type Latch

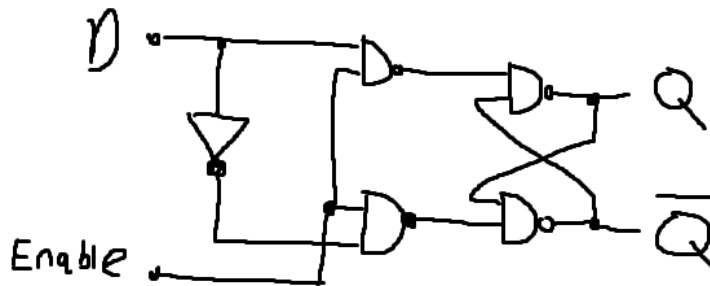


Figure 6: d-type latch

Below is the truth table for the d-type latch:

Enable	D	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	Q	\bar{Q}
1	0	0	1
1	1	1	0

Table 7: D-Type latch

- 15 Show how D-type latches can be arranged to form an N-bit register, explaining the function of your circuit.

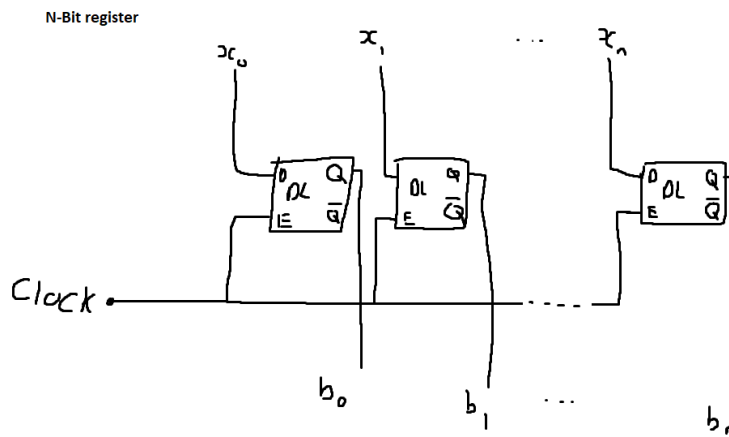


Figure 7: d-type latch

make note this diagram assumes the D-type latches are rising edge triggered.